

Department of Electrical and Computer Engineering COE328 – Digital Systems



Course Number:	COE328
Course Title:	Introduction Digital System
Semester/Year:	3/2023
Instructor:	
TA Name:	

Lab/Tutorial Report No.	
-------------------------	--

Report Title:	Design of a Simple General-Purpose Processor (GPU)
---------------	--

Section No.	
Group No.	
Submission Date:	12/ 3/ 23 by email
Due Date:	12/4/23

Student Name	Student ID	Signature*
Jonathan Ly	xxxx70138	

Table Of Contents:

Table Of Contents:	1
Introduction:	3
Components:	3
Description of Four Primary Components:	3
Latch 1/ Latch 2:	4
Block Diagram Screenshot:	4
Truth Table:	4
VHDL code/ Waveform:	5
Mealy FSM:	6
Block Diagram Screenshot:	6
Truth Table:	7
VHDL Code/ Waveform:	8
4 to 16 Decoder:	12
Block Diagram Screenshot:	12
Truth Table:	13
VHDL Code/ Waveform:	14
Seven Segment Display for GPU3 Only:	16
Block Diagram Screenshot:	16
Truth Table:	16
VHDL Code/ Waveform:	17
Seven Segment Display for GPU1, GPU2 & GPU3:	18
Block Diagram Screenshot:	18
Truth Table:	19
VHDL Code/ Waveform:	20
ALU1 Problem Set 1:	22
Description:	22
Block Schematic BDF Screenshot:	23
Table of decoder's Microcode & Result:	24
VHDL Code/ Waveform:	26
ALU2 Problem Set 2:	28
Description:	28
Block Schematic BDF Screenshot:	29
Table of decoder's Microcode & Result:	30
VHDL Code/ Waveform:	32
ALU3 Problem Set 3:	35
Description:	35
Block Schematic BDF Screenshot:	35
Table of decoder's Microcode & Result:	36

VHDL Code/ Waveform:	38
Conclusion:	41

Introduction:

The purpose of Lab 6 is to design and implement an Arithmetic and Logic Unit (ALU) using VHDL code and implement it on the FPGA board. A general processing unit (GPU) is composed of four distinct components. The Procuring Input Data, Storage Unit (Register), Control Unit and the ALU Core. The Procuring Input Data will consist of two 8-bit binary inputs called A and B which will go into the storage units. The Storage Units will be made up of two latches that will temporarily store A and B inputs that will be connected to the ALU core. The ALU core will perform the arithmetic and logical operations from the Storage Units and will output it to the Seven Segment Display Unit. The Control Unit is composed of a FSM block and 4 to 16 Decoder. The Control Unit will give instructions in the forms of Microcode, and each microcode will do a boolean operation (functions). The Control Unit will connect directly to the ALU core. All the components are connected using the same clock, so each rising edge, the components will receive the necessary inputs and instructions to obtain the outputs.

Components:

Description of Four Primary Components:

The Storage Units will consist of two Latches which temporarily store the input to be later used by the ASU core. It will receive eight bits binary input which is converted from our last four student numbers in hexadecimal. The last four digits of my student numbers are "0138", Latch 1 will receive 8-bit binary conversion of "01" (A) in hexadecimal and Latch 2 will receive 8-bit binary conversion of "38" (B) in hexadecimal. The FSM block is an up counter sequential circuit, which consists of 9 states. When it moves on a rising edge clock, the FSM will output the current state in 4-bit binary to the 4 to 16 Decoder which contains microcode in 16-bit binary, then the ALU will receive the microcode which tells which function to compute in order.

VHDL code/ Waveform:

Figure 1.1: Latch Code

```

1  LIBRARY ieee ;
2  USE ieee.std_logic_1164.all;
3  ENTITY latch1 IS
4  PORT ( A : IN STD_LOGIC_VECTOR(7 DOWNTO 0) ; -- 8 bit A input
5        Resetn, Clock : IN STD_LOGIC ; -- 1 bit clock input and 1 bit reset input bit
6        Q: OUT STD_LOGIC_VECTOR(7 DOWNTO 0)) ; -- 8 bit output
7  END latch1 ;
8  ARCHITECTURE Behavior OF latch1 IS
9  BEGIN
10 PROCESS ( Resetn, Clock ) -- Process takes reset and clock as inputs
11 BEGIN
12 IF Resetn = '1' THEN -- when reset input is '0' the latches does not operate
13   Q <= "00000000";
14 ELSIF Clock'EVENT AND Clock = '1' THEN -- level sensitive based on clock
15   Q <= A;
16 END IF;
17 END PROCESS;
18 END Behavior;
19

```

Figure 1.2: Wave form when Reset = 0


 


Figure 1.3: Wave form when Reset = 1

 


Description

The code for Latch 1 and Latch 2 are the same. Notice when Reset is 0, and clock is rising edge, the output will be whatever the input is. If Reset is 1, the output will always be zero in 8-bits.

Mealy FSM:

Block Diagram Screenshot:

 

VHDL Code/ Waveform:

Figure 2.1: FSM Mealy Code

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  entity Mealy0to8Upcounter is
4  port
5  (
6      clk: in std_logic;
7      data_in: in std_logic;
8      reset: in std_logic;
9      student_id: out std_logic_vector(3 downto 0);
10     current_state: out std_logic_vector(3 downto 0)
11 );
12 end entity;
13 architecture fsm of Mealy0to8Upcounter is
14
15     type state_type is (s0,s1,s2,s3,s4,s5,s6,s7,s8);
16
17     signal yfsm: state_type;
18
19 begin
20     process (clk,reset)
21     begin
22         if reset = '1' then
23             yfsm <= s0;
24         elsif (clk'EVENT AND clk = '1') then
25
26             case yfsm is --how FSM moves (upcounter, cycling through states 0 to 8 )
27             when s0 =>
28                 if (data_in = '1') then
29                     yfsm <= s1;
30                 elsif (data_in = '0') then
31                     yfsm <= s0;
32                 end if;
33
34             when s1 =>
35                 if (data_in = '1') then
36                     yfsm <= s2;
37                 elsif (data_in = '0') then
38                     yfsm <= s1;
39                 end if;
40
41             when s2 =>
42                 if (data_in = '1') then
43                     yfsm <= s3;
44
45                 elsif (data_in = '0')
46                 then
47                     yfsm <= s2;

```

```

48         end if;
49
50     when s3 =>
51         if (data_in = '1') then
52             yfsm <= s4;
53
54         elsif (data_in = '0') then
55             yfsm <= s3;
56         end if;
57
58     when s4 =>
59         if (data_in = '1') then
60             yfsm <= s5;
61         elsif (data_in = '0') then
62             yfsm <= s4;
63         end if;
64
65     when s5 =>
66         if (data_in = '1') then
67             yfsm <= s6;
68         elsif (data_in = '0') then
69             yfsm <= s5;
70         end if;
71
72     when s6 =>
73         if (data_in = '1') then
74             yfsm <= s7;
75         elsif (data_in = '0') then
76             yfsm <= s6;
77         end if;
78
79     when s7 =>
80         if (data_in = '1') then
81             yfsm <= s8;
82         elsif (data_in = '0') then
83             yfsm <= s7;
84         end if;
85
86     when s8 =>
87         if (data_in = '1') then
88             yfsm <= s0;
89         elsif (data_in = '0') then
90             yfsm <= s8;
91         end if;
92

```

```

93
94     end case;
95     end if;
96 end process;
97
98 process (yfsm, data_in)
99 begin
100     case yfsm is
101
102         when s0 => --at s0
103             current_state <= "0000"; --default current state
104             if (data_in = '1') then
105                 student_id <= "1000"; --8
106             elsif (data_in = '0') then
107                 student_id <= "0101"; --5
108             end if;
109
110         when s1 => --at s1
111             current_state <= "0001"; --default current state
112             if (data_in = '1') then
113                 student_id <= "0101"; --5
114             elsif (data_in = '0') then
115                 student_id <= "0000"; --0
116             end if;
117
118         when s2 => --at s2
119             current_state <= "0010"; --default current state
120             if (data_in = '1') then
121                 student_id <= "0000"; --0
122             elsif (data_in = '0') then
123                 student_id <= "0001"; --1
124             end if;
125
126         when s3 => --at s3
127             current_state <= "0011"; --default current state
128             if (data_in = '1') then
129                 student_id <= "0001"; --1
130             elsif (data_in = '0') then
131                 student_id <= "0001"; --1
132             end if;
133
134         when s4 => --at s4
135             current_state <= "0100"; --default current state
136             if (data_in = '1') then
137                 student_id <= "0001"; --1


```

```

138         elsif (data_in = '0') then
139             student_id <= "0111"; --7
140         end if;
141
142     when s5 => --at s5
143         current_state <= "0101"; --default current state
144         if (data_in = '1') then
145             student_id <= "0111"; --7
146         elsif (data_in = '0') then
147             student_id <= "0000"; --0
148         end if;
149
150     when s6 => --at s6
151         current_state <= "0110"; --default current state
152         if (data_in = '1') then
153             student_id <= "0000"; --0
154         elsif (data_in = '0') then
155             student_id <= "0001"; --1
156         end if;
157
158     when s7 => --at s7
159         current_state <= "0111"; --default current state
160         if (data_in = '1') then
161             student_id <= "0001"; --1
162         elsif (data_in = '0') then
163             student_id <= "0011"; --3
164         end if;
165
166     when s8 => --at s8
167         current_state <= "1000"; --default current state
168         if (data_in = '1') then
169             student_id <= "0011"; --3
170         elsif (data_in = '0') then
171             student_id <= "1000"; --8
172         end if;
173     end case;
174
175 end process;
176
177 end fsm;

```

Figure 2.2: Wave form when data_in = 1

 


Description

The waveform for data_in = 1 will match the truth table respective at each clock signal. We will never use when data_in = 0.

4 to 16 Decoder:

Block Diagram Screenshot:

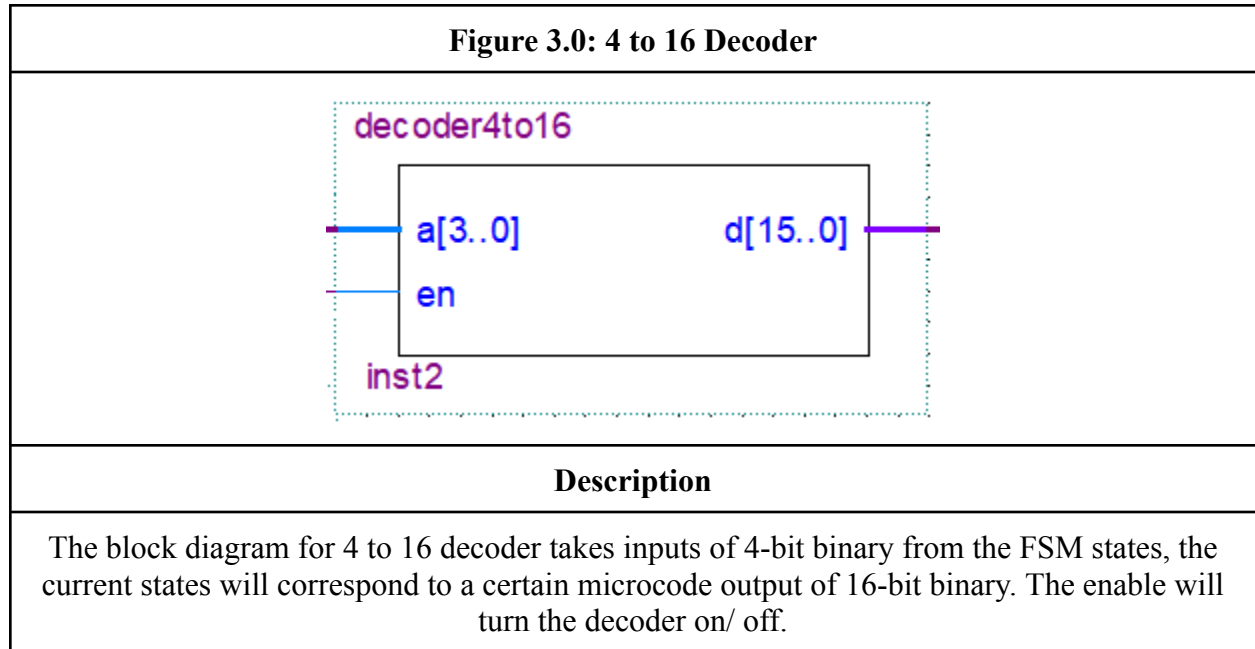

Truth Table:

Table 3.0: 4 to 16 Decoder	
Enable is 1: ON	
Input From FSM (4-bit Binary)	Output Decoder (16-bit Binary)
S0: 0000	0000000000000001
S1: 0001	0000000000000010
S2: 0010	0000000000000100
S3: 0011	0000000000001000
S4: 0100	0000000000010000
S5: 0101	0000000000100000
S6: 0110	0000000001000000
S7: 0111	0000000010000000
S8: 1000	0000000100000000
S9: dddd	dddddddddddddddd
.
S15: dddd	dddddddddddddddd
Description	
<p>When the decoder is on (enable is 1), the decoder will take inputs from the FSM (4-bit Binary) and the decoder will output (16-bit Binary). The 16 bit binary will be the microcode instruction for each function to run in the ALU core. We will not care about anything after state 9 to state 15 since we only have 9 functions for our GPU.</p>	

VHDL Code/ Waveform:

Figure 3.1: 4 to 16 Decoder Code

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  entity decoder4to16 is
4  port (a : in std_logic_vector(3 downto 0);
5       en : in std_logic;
6       d : out std_logic_vector(15 downto 0));
7  end decoder4to16;
8
9  architecture decoder of decoder4to16 is
10 begin
11     process (a)
12     begin
13         if (en = '0') then
14             d <= "0000000000000000";
15         else
16             case a is
17                 when "0000" => d <= "0000000000000001";
18                 when "0001" => d <= "0000000000000010";
19                 when "0010" => d <= "0000000000000100";
20                 when "0011" => d <= "0000000000001000";
21                 when "0100" => d <= "0000000000010000";
22                 when "0101" => d <= "0000000000100000";
23                 when "0110" => d <= "0000000001000000";
24                 when "0111" => d <= "0000000010000000";
25                 when "1000" => d <= "0000000100000000";
26                 when "1001" => d <= "0000001000000000";
27                 when "1010" => d <= "0000010000000000";
28                 when "1011" => d <= "0000100000000000";
29                 when "1100" => d <= "0001000000000000";
30                 when "1101" => d <= "0010000000000000";
31                 when "1110" => d <= "0100000000000000";
32                 when "1111" => d <= "1000000000000000";
33                 when others => d <= "0000000000000000";
34             end case;
35         end if;
36     end process;
37 end decoder;

```

Figure 3.2: Wave form when Enable = 1


 


Figure 3.3: Wave form when Enable = 0

 


Description

The code for Latch 1 and Latch 2 are the same. Notice when Reset is 0, and clock is rising edge, the output will be whatever the input is. If Reset is 1, the output will always be zero in 8-bits.

Seven Segment Display for GPU3 Only:

Block Diagram Screenshot:

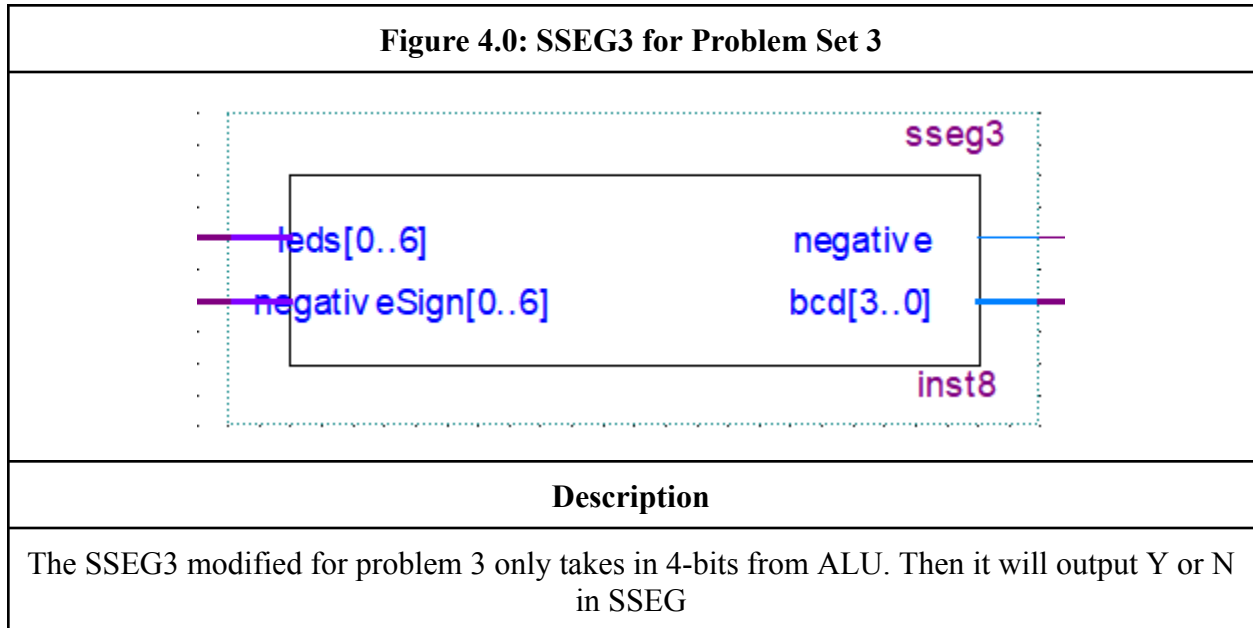

Truth Table:

Table 4.0: SSEG3		
Input	Output (abcdefg)	Y/N
0000	1110110	N
0001	0110011	Y
Description		
The modified SSEG3 only takes in 4-bit binary 0000 or 0001, 0000 will output a N in Seven Segment Code and 0001 will output a Y in Seven Segment Code.		

VHDL Code/ Waveform:


Figure 4.1: SSEG3 Code

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.all;
3
4  ENTITY sseg3 IS
5  PORT (negative : IN STD_LOGIC;
6        bcd : IN STD_LOGIC_VECTOR(3 DOWNT0 0);
7        leds, negativeSign: OUT STD_LOGIC_VECTOR(0 TO 6));
8  END sseg3;
9
10 ARCHITECTURE Behavior OF sseg3 IS
11 BEGIN
12     PROCESS (bcd)
13     BEGIN
14         if negative = '1' then
15             negativeSign <= "1111110";
16         else
17             negativeSign <= "1111111";
18
19         END if;
20
21         CASE bcd IS -- abcdefg
22             WHEN "0000" => leds <= "1110110"; -- n
23             WHEN "0001" => leds <= "0110011"; -- y
24             WHEN OTHERS => leds <= "-----";
25         END CASE;
26     END PROCESS;
27 END Behavior;

```

Figure 4.2: Waveform of SSEG3

 


Description

The code and waveforms will show Y or N depending on the input (output from ASU3). The negative component isn't connected and will not matter.

Seven Segment Display for GPU1, GPU2 & GPU3:

Block Diagram Screenshot:

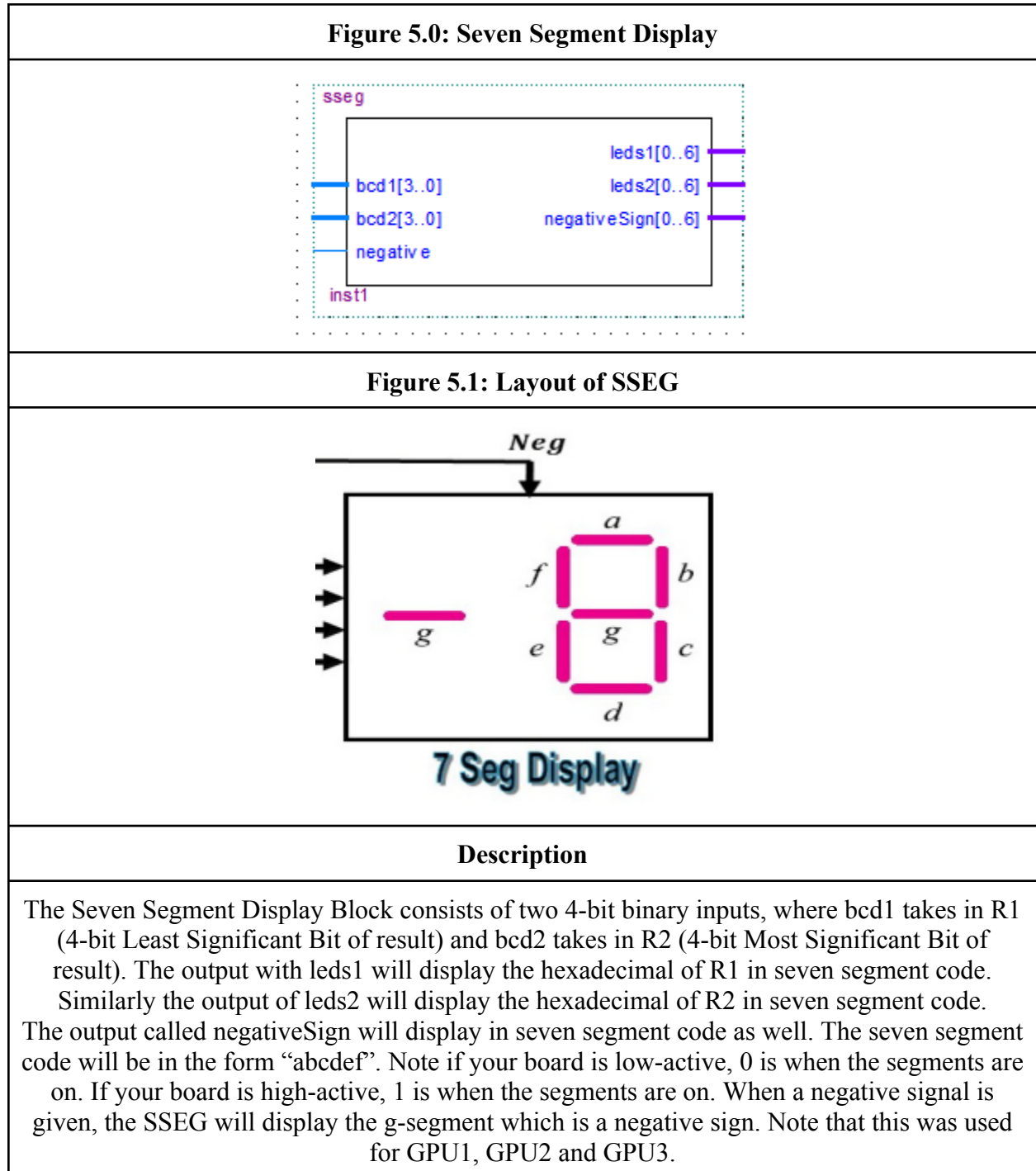

Truth Table:

Table 5.0: Seven Segments for high-active		
Negative (abcdefg)		
0000001		
Inputs (4-bit Binary)	Outputs (abcdefg: “1” means on)	Hexadecimal value
0000	0000000	0
0001	0110000	1
0010	1101101	2
0011	1111001	3
0100	0110011	4
0101	1011011	5
0110	1011111	6
0111	1110000	7
1000	1111111	8
1001	1110011	9
1010	1110111	A
1011	0011111	B
1100	0001101	C
1101	0111101	D
1110	1001111	E
1111	1000111	F
Description		
<p>Since our board was high-active, the 1 represents the segment being lit when it's on. The SSEG will display in hexadecimal. It takes in 4-bit binary input and it will display the values in hexadecimal on the SSEG. If the result is a negative number, it will display only the g-segment for a negative sign.</p>		

VHDL Code/ Waveform:

Figure 5.2: Seven Segment Display Code

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.all;
3
4  ENTITY sseg IS
5  PORT (
6      negative : IN STD_LOGIC;
7      bcd1 , bcd2 : IN STD_LOGIC_VECTOR(3 DOWNT0 0);
8      leds1, leds2, negativeSign: OUT STD_LOGIC_VECTOR(0 TO 6)
9  );
10 END sseg;
11
12 ARCHITECTURE Behavior OF sseg IS
13 BEGIN
14     PROCESS (negative)
15     BEGIN
16         IF negative = '1' THEN
17             negativeSign <= "0000001";
18
19         ELSE
20             negativeSign <= "0000000";
21
22         END IF;
23     END PROCESS;
24
25     PROCESS (bcd1)
26     BEGIN
27         CASE bcd1 IS -- abcdefg
28             WHEN "0000" => leds1 <= "1111110";
29             WHEN "0001" => leds1 <= "0110000";
30             WHEN "0010" => leds1 <= "1101101";
31             WHEN "0011" => leds1 <= "1111001";
32             WHEN "0100" => leds1 <= "0110011";
33             WHEN "0101" => leds1 <= "1011011";
34             WHEN "0110" => leds1 <= "1011111";
35             WHEN "0111" => leds1 <= "1110000";
36             WHEN "1000" => leds1 <= "1111111";
37             WHEN "1001" => leds1 <= "1110011";
38             WHEN "1010" => leds1 <= "1110110";
39             WHEN "1011" => leds1 <= "0011111";
40             WHEN "1100" => leds1 <= "0001101";
41             WHEN "1101" => leds1 <= "0111101";
42             WHEN "1110" => leds1 <= "1001111";
43             WHEN "1111" => leds1 <= "1000111";
44             WHEN OTHERS => leds1 <= "1001111";
45         END CASE;
46     END PROCESS;


```

```

47
48 PROCESS (bcd2)
49 BEGIN
50     CASE bcd2 IS -- abcdefg
51     WHEN "0000" => leds2 <= "1111110";
52     WHEN "0001" => leds2 <= "0110000";
53     WHEN "0010" => leds2 <= "1101101";
54     WHEN "0011" => leds2 <= "1111001";
55     WHEN "0100" => leds2 <= "0110011";
56     WHEN "0101" => leds2 <= "1011011";
57     WHEN "0110" => leds2 <= "1011111";
58     WHEN "0111" => leds2 <= "1110000";
59     WHEN "1000" => leds2 <= "1111111";
60     WHEN "1001" => leds2 <= "1110011";
61     WHEN "1010" => leds2 <= "1110110";
62     WHEN "1011" => leds2 <= "0011111";
63     WHEN "1100" => leds2 <= "0001101";
64     WHEN "1101" => leds2 <= "0111101";
65     WHEN "1110" => leds2 <= "1001111";
66     WHEN "1111" => leds2 <= "1000111";
67     WHEN OTHERS => leds2 <= "1001111";
68     END CASE;
69 END PROCESS;
70
71 END Behavior;

```

Figure 5.3: Waveform for Negative numbers

 

Description

The code is for a high-active SSEG board, where 1 in the SSEG is when the segment lights are on. When negative is 1, the negative SSEG will give g segment as 1. Which means the number in hexadecimal is negative.

ALU1 Problem Set 1:

Description:

The purpose of ALU1 is to compute the basic arithmetic and logical functions of 8-bit input A and 8-bit input B in binary from the Storage Unit which consists of two Latches. The Control Unit will give the microcode each time a new rising edge clock occurs. The microcode acts like an instruction to tell the ALU1 when to compute. The ALU will handle the computation when each microcode is called. The result of the computation is in 8-bit, but the SSEG only takes in 4-bit. The result will be broken down into R2 being the first four most significant bits and R1 being the last four Least Significant bits. There will be 3 SSEG which displays in hexadecimal format where the first one will display R2, the second will display R1 and finally the third will display the negative sign if the computation is a negative number (function 3 will have a negative output). Each microcode will have a different function associated (refer to Table 6.0). Each component of the GPU1 will be connected to the same clock. The output should be going along the FSM up counter which will have nine states for nine functions. After the 9 rising edge clock, it will start from the beginning and count up once more. When the reset of each component is pressed, it should go back to the beginning. Below I have attached the Block Schematic BDF Screenshot, the truth table of the expected output for each computation/ microcode instructions, the VHDL files, and finally the Waveforms.

Block Schematic BDF Screenshot:

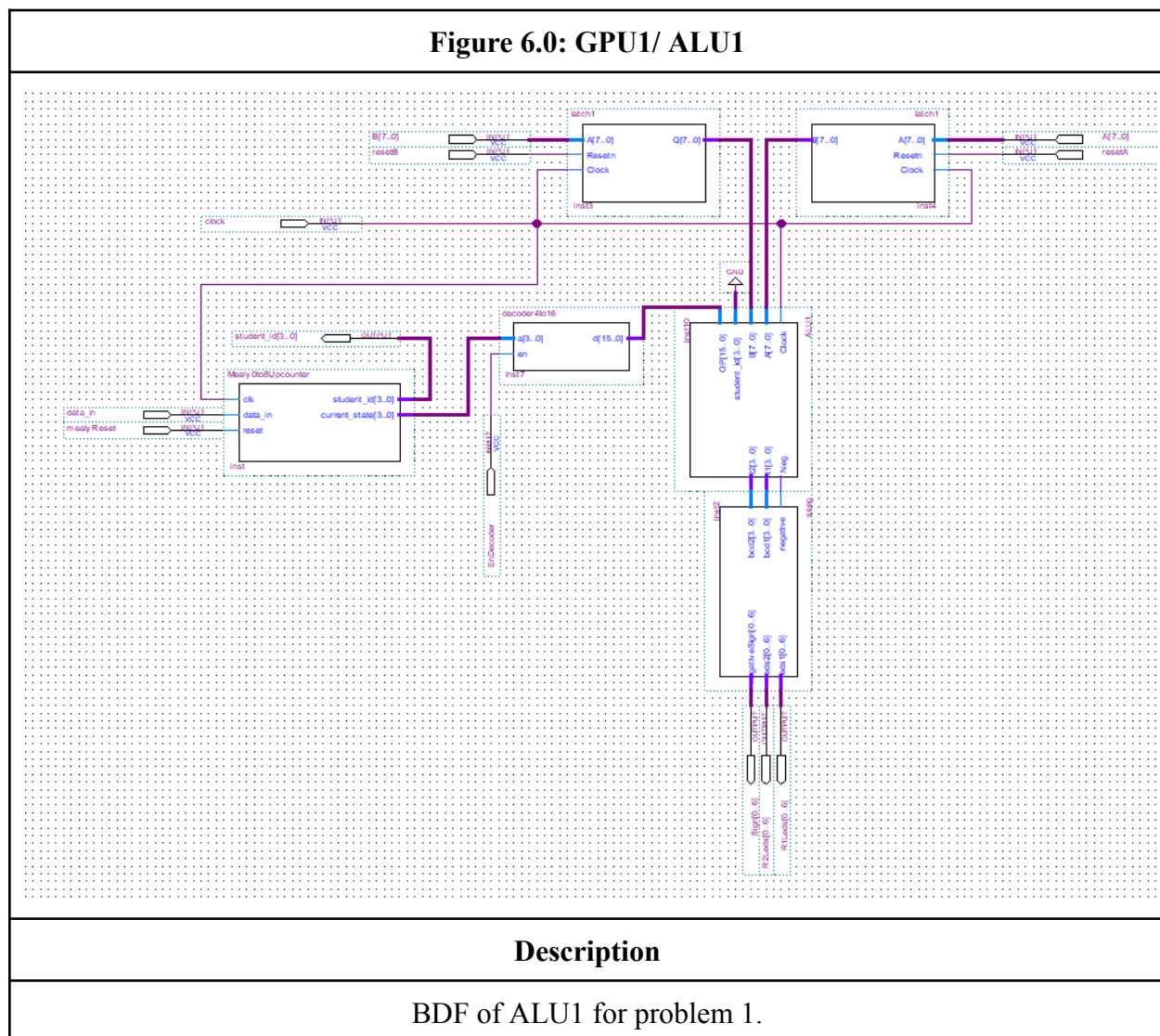


Table of decoder's Microcode & Result:

Table 6.0 Microcode for GPU1		
Function	Microcode (From Decoder)	Operation
1	0000000000000001	Sum(A,B)
2	0000000000000010	Diff(A,B)
3	0000000000000100	\overline{A}
4	0000000000001000	$\overline{A \cdot B}$
5	0000000000010000	$\overline{A + B}$
6	0000000000100000	$A \cdot B$
7	0000000001000000	$A \oplus B$
8	0000000010000000	$A + B$
9	0000000100000000	$\overline{A \oplus B}$
Description		
This table shows the microcode operation for GPU1 in ALU1 core. Each microcode corresponds to a specific function of arithmetic and logical computation.		

Table 6.1: Truth Table for Problem Set 1

Input of Latch1 (A)				Input of Latch2 (B)		
Hexadecimal	01			Hexadecimal	38	
Binary	00000001			Binary	00111000	
ASU1		Result in Binary		abcdefg		
Function #	Operation	Result 2	Result 1	SSEG2	SSEG1	Sign SSEG
1	Sum(A,B)	0011	1001	3: 1111001	9: 1110011	0000000
2	Diff(A,B)	0011	0111	3: 1111001	7: 1110000	0000001
3	\overline{A}	1111	1110	F: 1000111	E: 1001111	0000000
4	$\overline{A \bullet B}$	1111	1111	F: 1000111	F: 1000111	0000000
5	$\overline{A + B}$	1100	0110	C: 0001101	6: 1011111	0000000
6	$A \bullet B$	0000	0000	0: 1111110	0: 1111110	0000000
7	$A \oplus B$	0011	1001	3: 1111001	9: 1110011	0000000
8	$A + B$	0011	1001	3: 1111001	9: 1110011	0000000
9	$\overline{A \oplus B}$	1100	0110	C: 0001101	6: 1011111	0000000
Description						
This truth table shows the expected output from the SSEG in hexadecimal for each microcode function. The GPU will have output of Result2 (Four Most Significant Bit) and Result1 (Four Least Significant Bit).						

VHDL Code/ Waveform:

6.1: Code for ALU1

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_UNSIGNED.ALL;
4  use IEEE.NUMERIC_STD.ALL;
5  entity ALU1 is
6  port( Clock : in std_logic; -- input clock signal
7        A,B : in unsigned(7 downto 0); -- 8-bit inputs from latches A and B
8        student_id : in unsigned(3 downto 0); -- 4 bit student id from FSM
9        OP : in unsigned(15 downto 0); -- 16-bit selector for Operation from Decoder
10       Neg: out std_logic; -- is the result negative ? Set-ve bit output
11       R1 : out unsigned(3 downto 0); -- lower 4-bits of 8-bit Result Output
12       R2 : out unsigned(3 downto 0)); -- higher 4-bits of 8-bit Result Output
13
14  end ALU1;
15  architecture calculation of ALU1 is -- temporary signal declarations.
16  signal Reg1,Reg2,Result : unsigned(7 downto 0) := (others => '0');
17  signal Reg4 : unsigned (0 to 7);
18  begin
19  Reg1 <= A; -- temporarily store A in Reg1 local variable
20  Reg2 <= B; -- temporarily store B in Reg2 local variable
21
22  process(Clock, OP)
23  begin
24  if(rising_edge(Clock)) THEN -- Do the calculation @ positive edge of clock cycle.
25  case OP is
26
27  WHEN "0000000000000001"=>
28  -- Do Addition for Reg1 and Reg2
29  Result <= Reg1 + Reg2;
30  Neg <= '0';
31
32  when "0000000000000010" =>
33  if Reg1<Reg2 then
34  Result <= Reg2 - Reg1;
35  neg <= '1';
36  else
37  Result <= Reg1 - Reg2;
38  neg <= '0';
39  end if;
40
41  WHEN "0000000000000100"=>
42  --Do Inverse
43  Result <= NOT Reg1;
44  Neg <= '0';
45


```

```

45
46     WHEN "0000000000001000"=>
47         -- Do Boolean NAND
48         Result <= NOT(Reg1 AND Reg2);
49         Neg <= '0';
50
51     WHEN "0000000000010000"=>
52         -- Do Boolean NOR
53         Result <= NOT(Reg1 OR Reg2);
54         Neg <= '0';
55
56     WHEN "0000000000100000"=>
57         -- Do Boolean AND
58         Result <= Reg1 AND Reg2;
59         Neg <= '0';
60
61     WHEN "0000000001000000"=>
62         -- Do Boolean OR
63         Result <= Reg1 OR Reg2;
64         Neg <= '0';
65
66     WHEN "0000000010000000"=>
67         -- Do Boolean XOR
68         Result <= Reg1 XOR Reg2;
69         Neg <= '0';
70
71     WHEN "0000000100000000"=>
72         -- Do Boolean XNOR
73         Result <= Reg1 XNOR Reg2;
74         Neg <= '0';
75
76     WHEN OTHERS =>
77         -- Don't care, do nothing
78         end case;
79     end if;
80 end process;
81 R1 <= Result(3 downto 0); -- Since the output seven segments can
82 R2 <= Result(7 downto 4); -- only 4-bits, split the 8-bit to two 4-bits.
83 end calculation;

```

Figure 6.2: Waveform of GPU1

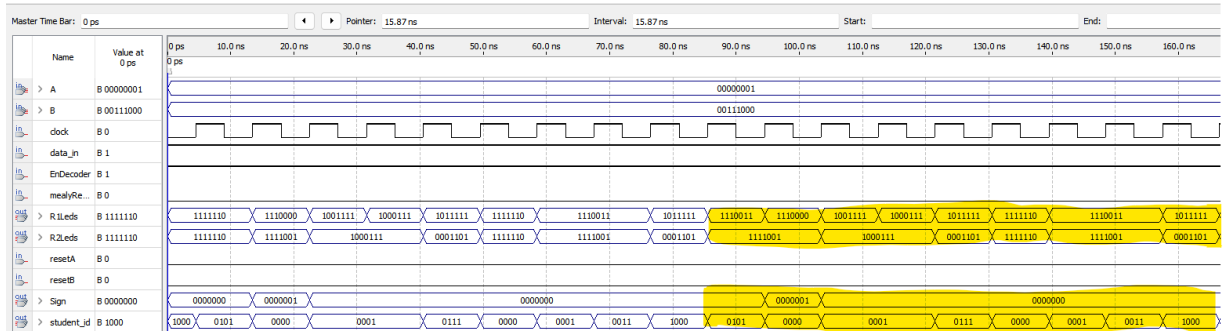

Description

Note that the output is correct in the yellow highlighted region. Sign, R2Leds, R1Leds outputs are in terms of SSEG code where 1 means lit on SSEG and 0 means off in SSEG. Recall that the format for SSEG is abcdef, which corresponds to the Seven Segments on/off in SSEG. student_id is in the binary of student number. The first function should be

ALU2 Problem Set 2:

Description:

The workings of ALU2 is very similar to ALU1 which was used to compute the basic arithmetic and logical functions of 8-bit input A and 8-bit input B in binary from the Storage Unit which consists of two Latches. Just for GPU1, the Control Unit will also give the microcode each time a new rising edge clock occurs. The microcode acts like an instruction to tell the ALU2 when to compute. The ALU2 will handle the computation when each microcode is called. The result of the computation is in 8-bit, but the SSEG only takes in 4-bit. The result will be broken down into R2 being the first four most significant bits and R1 being the last four Least Significant bits. There will be 2 SSEG which display in hexadecimal format where the first one will display R2, the second will display R1. Each microcode will have a different function associated (refer to Table 7.0). Each component of the GPU2 will be connected to the same clock. The output should be going along the FSM up counter which will have nine states for nine functions. After the 9 rising edge clock, it will start from the beginning and count up once more. When the reset of each component is pressed, it should go back to the beginning. Below I have attached the Block Schematic BDF Screenshot, the truth table of the expected output for each computation/ microcode instructions, the VHDL files, and finally the Waveforms. Note that we did part g for the problem set.

Figure 7.0: GPU2/ ALU2

Description

BDF of ALU2 for problem 2.

BDF of ALU2 for problem 2.

BDF of ALU2 for problem 2.

Table of decoder's Microcode & Result:

Table 7.0: Microcode for ALU2 (g)		
Function	Microcode (From Decoder)	Operation
1	0000000000000001	Invert Significant-bit A
2	0000000000000010	SHL A by 4, all 1 after
3	0000000000000100	Invert Upper 4-bit B
4	0000000000001000	Min(A, B)
5	0000000000010000	Sum(A,B) add 4
6	0000000000100000	A add 3
7	0000000001000000	Print A when Even-bits of A becomes Even-bits of B
8	0000000010000000	$\overline{A \oplus B}$
9	0000000100000000	ROR B by 3 bits
Description		
This table shows the microcode operation for GPU2 in ALU2 core. Each microcode corresponds to a specific function of arithmetic and logical computation.		

Table 7.1: Table Truth Table for Problem Set 2 (g)					
Input of Latch1 (A)			Input of Latch2 (B)		
Hexadecimal	01		Hexadecimal	38	
Binary	00000001		Binary	00111000	
ASU2		Result in Binary		abcdefg	
Function #	Operation	Result 2	Result 1	SSEG2	SSEG1
1	Invert Significant-bit A	1000	0000	8: 1111111	0: 1111110
2	SHL A by 4, all 1 after	0001	1111	1: 0110000	F: 1000111
3	Invert Upper 4-bit B	1100	1000	C: 0001101	8: 1111111
4	Min(A, B)	0000	0001	0: 1111110	1: 0110000
5	Sum(A,B) add 4	0010	1011	3: 1111001	D: 0111101
6	A add 3	0000	0100	0: 1111110	4: 0110011
7	Print A when Even-bits of A becomes Even-bits of B	0001	0000	1: 0110000	0: 1111110
8	$\overline{A \oplus B}$	1100	0110	C: 0001101	6: 1011111
9	ROR B by 3 bits	0000	0111	0: 1111110	7: 1110000
Description					
This truth table shows the expected output from the SSEG in hexadecimal for each microcode function. The GPU will have output of Result2 (Four Most Significant Bit) and Result1 (Four Least Significant Bit).					

VHDL Code/ Waveform:

Figure 7.1: Code for ALU2

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_UNSIGNED.ALL;
4  use IEEE.NUMERIC_STD.ALL;
5  entity ALU2 is
6  port( Clock : in std_logic; -- input clock signal
7      A,B : in unsigned(7 downto 0); -- 8-bit inputs from latches A and B
8      student_id : in unsigned(3 downto 0); -- 4 bit student id from FSM
9      OP : in unsigned(15 downto 0); -- 16-bit selector for Operation from Decoder
10     Neg: out std_logic; -- is the result negative ? Set-ve bit output
11     R1 : out unsigned(3 downto 0); -- lower 4-bits of 8-bit Result Output
12     R2 : out unsigned(3 downto 0)); -- higher 4-bits of 8-bit Result Output
13 end ALU2;
14 architecture calculation of ALU2 is -- temporary signal declarations.
15     signal Reg1,Reg2,Result : unsigned(7 downto 0) := (others => '0');
16     signal Reg4 : unsigned (0 to 7);
17 begin
18     Reg1 <= A; -- temporarily store A in Reg1 local variable
19     Reg2 <= B; -- temporarily store B in Reg2 local variable
20     process(Clock, OP)
21     begin
22         if(rising_edge(Clock)) THEN -- Do the calculation @ positive edge of clock cycle.
23             case OP is
24                 WHEN "0000000000000001" =>
25                     Result(0)<= Reg1(7);
26                     Result(1)<= Reg1(6);
27                     Result(2)<= Reg1(5);
28                     Result(3)<= Reg1(4);
29                     Result(4)<= Reg1(3);
30                     Result(5)<= Reg1(2);
31                     Result(6)<= Reg1(1);
32                     Result(7)<= Reg1(0);
33                     --Neg<='0';
34
35                 WHEN "0000000000000010" =>
36
37                     Result<= Reg1 sll 4; --note was 3
38                     Result(0)<='1';
39                     Result(1)<='1';
40                     Result(2)<='1';
41                     Result(3)<='1';
42


```

```

44      WHEN "000000000000100" =>
45          Result(7) <= Not Reg2(7);
46          Result(6) <= Not Reg2(6);
47          Result(5) <= Not Reg2(5);
48          Result(4) <= Not Reg2(4);
49          Result(3) <= Reg2(3);
50          Result(2) <= Reg2(2);
51          Result(1) <= Reg2(1);
52          Result(0) <= Reg2(0);
53
54
55      WHEN "0000000000001000" =>
56          if(Reg1 <= Reg2) then
57              Result <= Reg1;
58          else
59              Result <= Reg2;
60          end if;
61
62      WHEN "0000000000010000" => Result <= Reg1 + Reg2 + "00000100"; --note before was 4
63
64      WHEN "0000000000100000" => Result <= Reg1 + "00000011";
65
66      WHEN "0000000001000000" =>
67
68          Result(0) <= Reg2(0);
69          Result(1) <= Reg1(1);
70          Result(2) <= Reg2(2);
71          Result(3) <= Reg1(3);
72          Result(4) <= Reg2(4);
73          Result(5) <= Reg1(5);
74          Result(6) <= Reg2(6);
75          Result(7) <= Reg1(7);
76
77
78      WHEN "0000000010000000" => Result <= (Reg1 XNOR Reg2);
79
80      WHEN "0000000100000000" => Result <= Reg2 ROR 3;
81
82      WHEN OTHERS =>
83          Result <= "-----";
84
85
86      end case;
87  end if;
88  end process;
89
90  R1 <= Result(3 downto 0); -- Since the output seven segments can
91  R2 <= Result(7 downto 4); -- only 4-bits, split the 8-bit to two 4-bits.
92  end calculations;

```

Figure 7.2: Waveform of GPU2

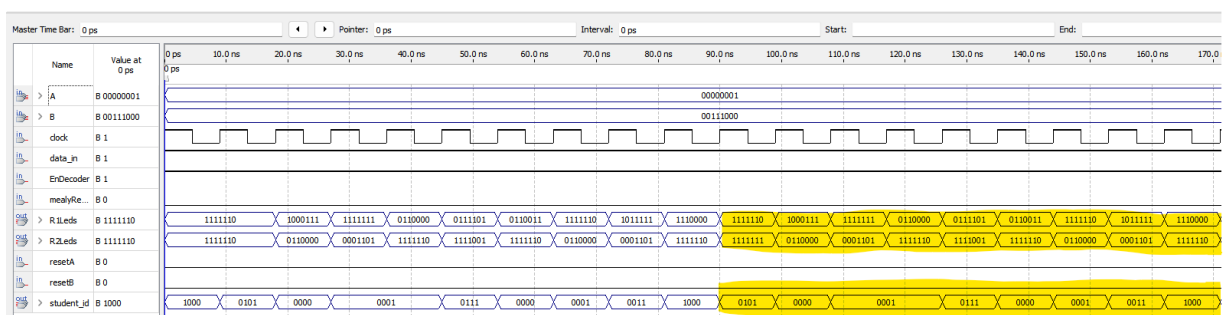

Description

Note that the output is correct in the yellow highlighted region. Sign, R2Leds, R1Leds outputs

are in terms of SSEG code where 1 means lit on SSEG and 0 means off in SSEG. Recall that the format for SSEG is abcdef, which corresponds to the Seven Segments on/off in SSEG. student_id is in the binary of student number.

ALU3 Problem Set 3:

Description:

In problem set 3, the GPU will still contain the 4 primary components. The main difference of ALU3 is that the microcode functions are different. The methods of retrieving inputs are still the same (retrieved from the Storage Unit) and retrieving the microcontroller is also the same (retrieved from the Control Unit). The output of ALU3 will also be in 4-bits but it will be acquired from the least significant bit of 00000000 when the comparison is false and 00000001 when comparison is true which depends on the function detailed in Table 8.0. The ALU will only output the 4-bits which SSEG3 will output in the display either a Y or N in SSEG code (refer to Table 8.1). The details of functionalities and outputs of the GPU3 will be shown below. Note that we did part g of the problem set.

Block Schematic BDF Screenshot:

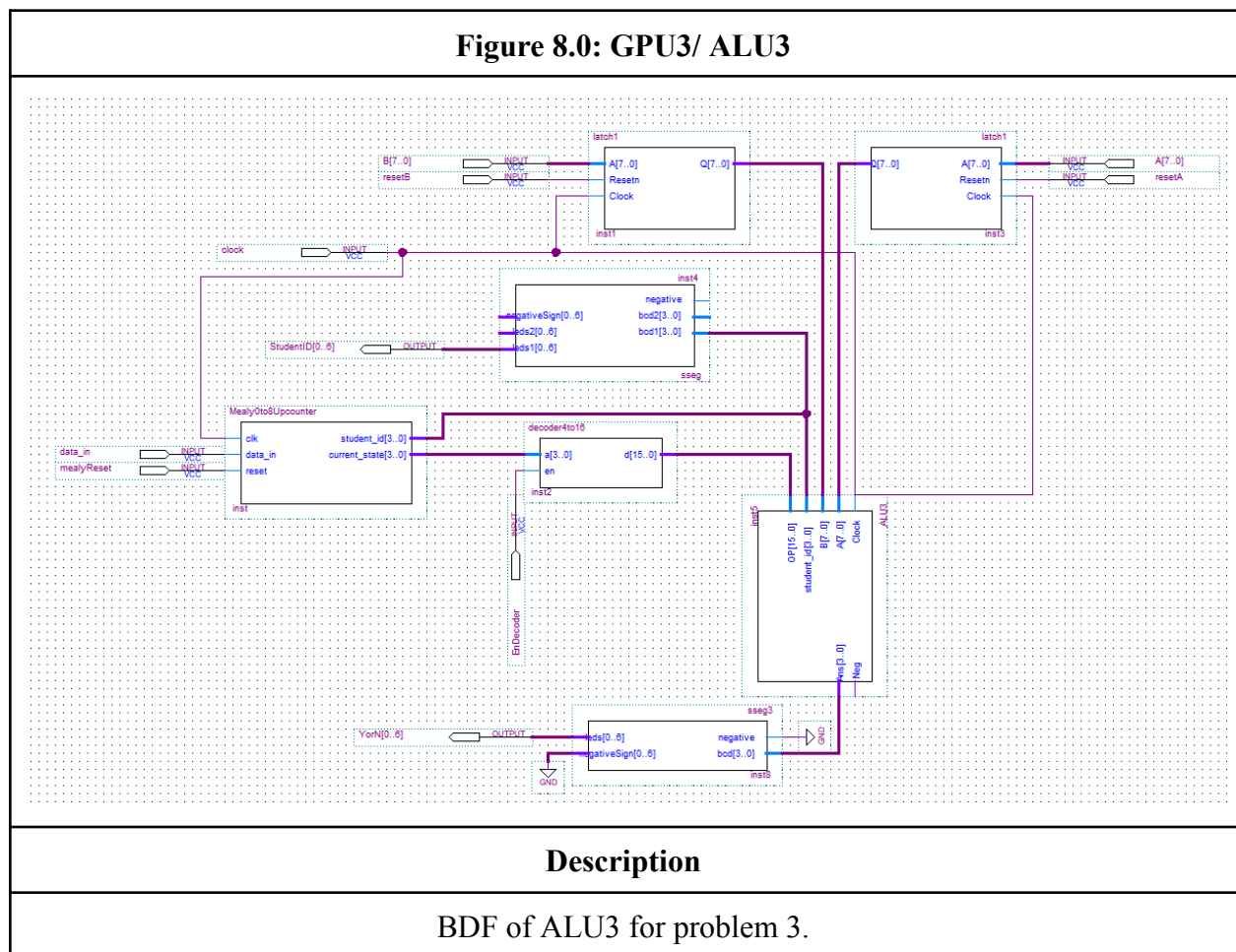


Table of decoder's Microcode & Result:

Table 8.0: Microcode of ASU3 (g)		
Function	Microcode (From Decoder)	Operation
1	0000000000000001	Compare the 1st of student number with both bits of A in hexadecimal
2	0000000000000010	Compare the 2nd of student number with both bits of A in hexadecimal
3	0000000000000100	Compare the 3rd number of student number with both bits of A in hexadecimal
4	0000000000001000	Compare the 4th number of student number with both bits of A in hexadecimal
5	0000000000010000	Compare the 5th number of student number with both bits of A in hexadecimal
6	0000000000100000	Compare the 6th number of student number with both bits of A in hexadecimal
7	0000000001000000	Compare the 7th number of student number with both bits of A in hexadecimal
8	0000000010000000	Compare the 8th number of student number with both bits of A in hexadecimal
9	0000000100000000	Compare the 9th number of student number with both bits of A in hexadecimal
Description		
This table shows the microcode operation for GPU3 in ALU3 core. Each microcode corresponds to a specific function of arithmetic and logical computation.		

Table: 8.1: Truth Table for Problem Set 3 (g)					
Input of Latch1 (A) ONLY					
Hexadecimal			01		
Binary			00000001		
ASU3		A in Binary		SSEG	
Function #	Student ID	First 4-bits	Last 4-bits	abcdefg	Y or N
1	5: 0101	0000	0001	1110110	N
2	0: 0000	0000	0001	0110011	Y
3	1: 0001	0000	0001	0110011	Y
4	1: 0001	0000	0001	0110011	Y
5	7: 0111	0000	0001	1110110	N
6	0: 0000	0000	0001	0110011	Y
7	1: 0001	0000	0001	0110011	Y
8	3: 0011	0000	0001	1110110	N
9	8: 1000	0000	0001	1110110	N
Description					
When the ALU3 checks for current state, it will check for the first 4 bits of A (MSB) and check for the last 4 bits of A (LSB). If one of them matches the 4 bit student number, it will output 0000 or 0001 from ALU3. The SSEG3 will take in 0000 or 0001 and give Y for 0001 or N for 0000.					

VHDL Code/ Waveform:

Figure 8.1: Code for ALU2

```

1  LIBRARY IEEE;
2  USE IEEE.STD_LOGIC_1164.all;
3  USE IEEE.STD_LOGIC_UNSIGNED.all;
4  USE IEEE.NUMERIC_STD.all;
5  ENTITY ALU3 IS
6  PORT (Clock: IN STD_LOGIC;
7        A, B: IN UNSIGNED(7 DOWNTO 0);
8        student_id: IN UNSIGNED(3 DOWNTO 0);
9        OP: IN UNSIGNED(15 DOWNTO 0);
10       Neg: OUT STD_LOGIC;
11       Ans: OUT UNSIGNED(3 DOWNTO 0));
12
13  END ALU3;
14
15  ARCHITECTURE calculation of ALU3 IS
16  SIGNAL Reg1, Reg2, Result: UNSIGNED(7 DOWNTO 0) := (OTHERS => '0');
17  SIGNAL Reg4: UNSIGNED (0 TO 7);
18  BEGIN
19
20     Reg1 <= A;
21     Reg2 <= B;
22
23  PROCESS (Clock, OP)
24  BEGIN
25  CASE OP IS
26  WHEN "0000000000000001" =>
27  if (Reg1(3 downto 0) = student_id) then
28  Result <= "00000001";
29  elsif (Reg1(7 downto 4) = student_id) then
30  Result <= "00000001";
31  else
32  Result <= "00000000";
33  end if;
34
35  WHEN "0000000000000010" =>
36  if (Reg1(3 downto 0) = student_id) then
37  Result <= "00000001";
38  elsif (Reg1(7 downto 4) = student_id) then
39  Result <= "00000001";
40  else
41  Result <= "00000000";
42  end if;
43
44
45  WHEN "0000000000000100" =>
46  if (Reg1(3 downto 0) = student_id) then

```

```

44
45 WHEN "00000000000000100" =>
46   if (Reg1(3 downto 0) = student_id) then
47     Result <= "00000001";
48   elsif (Reg1(7 downto 4) = student_id) then
49     Result <= "00000001";
50   else
51     Result <= "00000000";
52   end if;
53
54 WHEN "0000000000001000" =>
55   if (Reg1(3 downto 0) = student_id) then
56     Result <= "00000001";
57   elsif (Reg1(7 downto 4) = student_id) then
58     Result <= "00000001";
59   else
60     Result <= "00000000";
61   end if;
62
63 WHEN "0000000000010000" =>
64   if (Reg1(3 downto 0) = student_id) then
65     Result <= "00000001";
66   elsif (Reg1(7 downto 4) = student_id) then
67     Result <= "00000001";
68   else
69     Result <= "00000000";
70   end if;
71
72 WHEN "0000000000100000" =>
73   if (Reg1(3 downto 0) = student_id) then
74     Result <= "00000001";
75   elsif (Reg1(7 downto 4) = student_id) then
76     Result <= "00000001";
77   else
78     Result <= "00000000";
79   end if;

```




```

80
81 WHEN "0000000010000000" =>
82   if (Reg1(3 downto 0) = student_id) then
83     Result <= "00000001";
84   elsif (Reg1(7 downto 4) = student_id) then
85     Result <= "00000001";
86   else
87     Result <= "00000000";
88   end if;
89
90 WHEN "0000000010000000" =>
91   if (Reg1(3 downto 0) = student_id) then
92     Result <= "00000001";
93   elsif (Reg1(7 downto 4) = student_id) then
94     Result <= "00000001";
95   else
96     Result <= "00000000";
97   end if;
98
99 WHEN "0000000100000000" =>
100   if (Reg1(3 downto 0) = student_id) then
101     Result <= "00000001";
102   elsif (Reg1(7 downto 4) = student_id) then
103     Result <= "00000001";
104   else
105     Result <= "00000000";
106   end if;
107
108 WHEN OTHERS =>
109   Result <= "-----";
110
111 END CASE;
112 END PROCESS;
113
114 Ans <= Result(3 downto 0);
115
116 END calculation;

```

Figure 8.2: Waveform of GPU3

 

Description

Since our first mealy state would be the student number of 8, it will print 8 in hexadecimal in the SSEG.

Conclusion:

Overall, in Lab 6 we were able to design and program in VHDL of a General-Purpose Processor Unit (GPU). We are able to finalize what we learn throughout the semester to compute arithmetic and logical operations in the ALU. I understood the importance of the 4 components which make up the GPU. Without them, we would not be able to perform the operation. The GPU can perform multiple tasks from only 2 inputs from the user once. Without the Storage unit, which acts as a place to store the inputs (which acts as the memory for the ALU), the ALU will not be able to access them again and again after completing one function after another. The control unit was also very important since it gave the instructions for the ALU when to conduct the operation. The importance of the clock signal to be synchronized in each component is very crucial since without it, the ALU and its main components will not be able to move from one function to another. With the basic understanding of how the GPU works, I can imagine the possibilities that logical systems can do to perform certain tasks to improve the efficiency in day to day tasks.